

# Gate Assignment 2

Vijay Varma - AI20BTECH11012

Download latex-tikz codes from

[https://github.com/KBVijayVarma/EE3900/tree/main/Gate\\_Assignment\\_2](https://github.com/KBVijayVarma/EE3900/tree/main/Gate_Assignment_2)

above,

## PROBLEM (GATE EC-2008 Q 78)

In the following network, the switch is closed at  $t = 0$  and the sampling starts from  $t = 0$ . The sampling frequency is 10Hz.

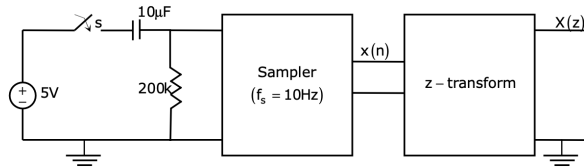


Fig. 0: question

The samples  $x(n)$  ( $n = 0, 1, 2, \dots$ ) are given by

- 1)  $5(1 - e^{-0.05n})$
- 2)  $5e^{-0.05n}$
- 3)  $5(1 - e^{-5n})$
- 4)  $5e^{-5n}$

## SOLUTION

The charge  $q$ , current  $i$ , voltage  $V$  in a circuit are,

$$q = cV \quad (0.0.1)$$

$$i = \frac{dq}{dt} = c \frac{dV}{dt} \quad (0.0.2)$$

$$i = \frac{V}{R} \quad (0.0.3)$$

$$\therefore c \frac{dV}{dt} = \frac{V}{R} \quad (0.0.4)$$

In the given circuit, let  $V(t)$  be the voltage at a given time  $t$ . Converting all variables into  $s$  domain, From

$$\frac{-V(s) + \frac{5}{s}}{\frac{1}{sC}} = \frac{V(s)}{R} \quad (0.0.5)$$

$$\frac{5}{sV(s)} - 1 = \frac{1}{sRc} \quad (0.0.6)$$

$$V(s) = \frac{5}{s(1 + \frac{1}{sRc})} \quad (0.0.7)$$

$$V(s) = \frac{5}{s + \frac{1}{Rc}} \quad (0.0.8)$$

Now applying Inverse Laplace Transform we get,

$$V(t) = 5e^{-\frac{t}{Rc}} \quad (0.0.9)$$

Substituting the values of

$$R = 200K = 2 \times 10^5 \Omega \quad (0.0.10)$$

$$c = 10\mu F = 10^{-5} F \quad (0.0.11)$$

$$Rc = 2 \quad (0.0.12)$$

We get

$$V(t) = 5e^{-\frac{t}{2}} = 5e^{-0.5t} \quad (0.0.13)$$

Now, given Sampling frequency  $f = 10$  Hz.

Sampling period  $T$  is given by

$$T = \frac{1}{f} = 0.1s \quad (0.0.14)$$

Now, samples  $x[n]$  are obtained by replacing  $t$  with  $nT$  in (0.0.13),

$$x[n] = 5e^{-0.5nT} \quad (0.0.15)$$

$$x[n] = 5e^{-0.05n} \quad (0.0.16)$$

The samples  $x(n)$  ( $n = 0, 1, 2, \dots$ ) are given by  $x[n] = 5e^{-0.05n}$ .

Hence, the correct answer is **Option 2**.