

Gate Assignment 2

Vijay Varma - AI20BTECH11012

Download latex-tikz codes from

https://github.com/KBVijayVarma/EE3900/tree/main/Gate_Assignment_2

PROBLEM (GATE EC-2008 Q 78)

In the following network, the switch is closed at $t = 0$ and the sampling starts from $t = 0$. The sampling frequency is 10Hz.

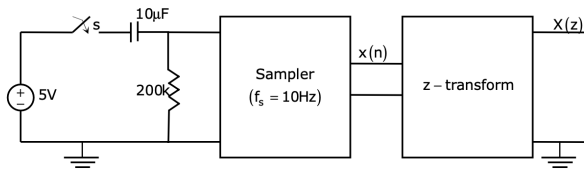


Fig. 0: question

The samples $x(n)$ ($n = 0, 1, 2, \dots$) are given by

- 1) $5(1 - e^{-0.05n})$
- 2) $5e^{-0.05n}$
- 3) $5(1 - e^{-5n})$
- 4) $5e^{-5n}$

SOLUTION

The charge q , current i , voltage V in a circuit are,

$$q = cV \quad (0.0.1)$$

$$i = \frac{dq}{dt} = c \frac{dV}{dt} \quad (0.0.2)$$

$$i = \frac{V}{R} \quad (0.0.3)$$

$$\therefore c \frac{dV}{dt} = \frac{V}{R} \quad (0.0.4)$$

In the given circuit, let V be the voltage at a given time t . From above,

$$c \frac{d(5 - V)}{dt} = \frac{V}{R} \quad (0.0.5)$$

$$-c \frac{dV}{dt} = \frac{V}{R} \quad (0.0.6)$$

$$\frac{dV}{V} = -\frac{dt}{Rc} \quad (0.0.7)$$

Integrating on both sides,

$$[\ln V]_5^V = -\frac{1}{Rc} [t]_0^t \quad (0.0.8)$$

$$\ln \frac{V}{5} = -\frac{t}{Rc} \quad (0.0.9)$$

$$\frac{V}{5} = e^{-\frac{t}{Rc}} \quad (0.0.10)$$

$$V = 5e^{-\frac{t}{Rc}} \quad (0.0.11)$$

Substituting the values of

$$R = 200K = 2 \times 10^5 \Omega \quad (0.0.12)$$

$$c = 10\mu F = 10^{-5} F \quad (0.0.13)$$

$$Rc = 2 \quad (0.0.14)$$

We get

$$V = 5e^{-\frac{t}{2}} = 5e^{-0.5t} \quad (0.0.15)$$

Now, given Sampling frequency $f = 10$ Hz.

Sampling period T is given by

$$T = \frac{1}{f} = 0.1s \quad (0.0.16)$$

Now, samples $x[n]$ are obtained by replacing t with nT in (0.0.15),

$$x[n] = 5e^{-0.5nT} \quad (0.0.17)$$

$$x[n] = 5e^{-0.05n} \quad (0.0.18)$$

The samples $x(n)$ ($n = 0, 1, 2, \dots$) are given by $x[n] = 5e^{-0.05n}$.

Hence, the correct answer is **Option 2**.